

# OP-AMPS

Review Ideal Op-Amps  
And  
Begin Inverting Amplifiers


## Review

- ▣ High open-loop gain and negative feedback forces differential input voltage to be zero
- ▣ High input resistance forces input current to be zero
- ▣ Use these assumptions to analyze the closed-loop gain

Sidenote: Office hour 1-2 pm on Fridays in Cobleigh 539, except today it will be from 2-3 pm.
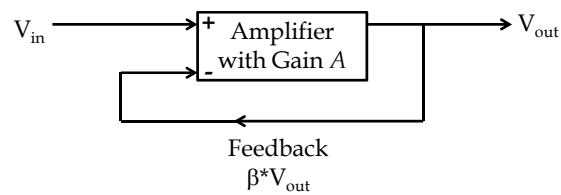
## Review of Negative Feedback

- Feedback – signal or voltage from output is superimposed on input
  - Typically done to achieve a desired performance




EELE 250/Fall 2011

Montana State University

Sarah Lukes 3

## Gain

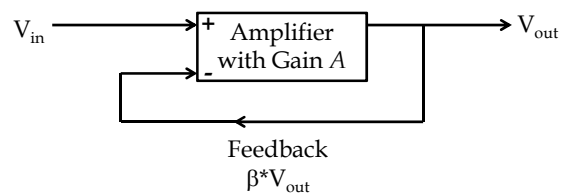

- With Feedback our gain is no longer just the open-loop gain  $A$  of the amplifier or  $Gain_{OL} = \frac{V_{out}}{V_{in}} = A$ 
  - We know  $V_{out} = A * (V_{in} - \beta V_{out})$
  - Rearrange to find  $Gain_{negfeedback} = \frac{V_{out}}{V_{in}} = \frac{A}{1 + A\beta}$

EELE 250/Fall 2011

Montana State University

Sarah Lukes 4


## Summing-point constraint

- With a negative feedback system, the feedback ensures that the output voltage of the ideal op-amp is the value required to force
  - The differential input voltage to zero
  - The input current to zero

## I-clicker Question

- The wire connecting the output of the op-amp to the input should be connected to the
  - a) noninverting (+) input
  - b) inverting (-) input
  - c) both inputs
  - d) either input - they are essentially the same
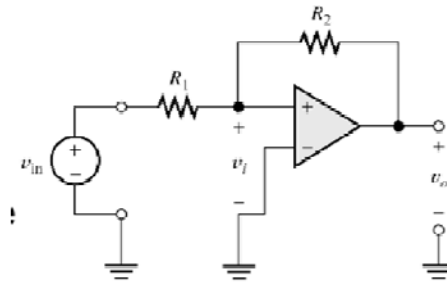
## What happens if we have positive feedback?



- The input and output voltages increase in magnitude until the output voltage reaches one of its extremes (limited by power supply).

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Fifth Edition, by Allan R. Hambley, ©2011 Pearson Education, Inc.  
 EELE 250/Fall 2011 Montana State University Sarah Lukes 7

## Steps to analyze an ideal op-amp circuit


- Verify that negative feedback is present
- Assume the differential input voltage and input current are forced to zero
- Apply standard circuit-analysis principles, such as Kirchoff's and Ohm's laws to solve.

EELE 250/Fall 2011

Montana State University

Sarah Lukes 8

## Basic Inverter

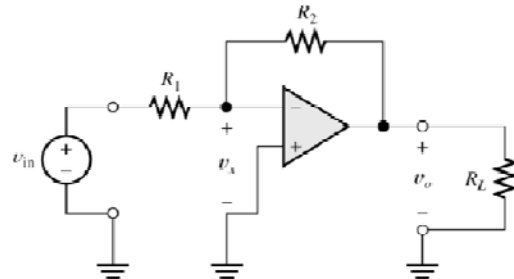

Closed Loop Gain

$$A_v = \frac{v_o}{v_{in}} = -\frac{R_2}{R_1}$$

- ▣ It is negative and only depends on R1 and R2.
- ▣ It does not depend on RL.
- ▣ Inverter: input impedance  $Z_{in} = v_{in} / i_1 = R1$   
output impedance = 0

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Fifth Edition, by Allan R. Hambley, ©2011 Pearson Education, Inc

ELE 250/Fall 2011

Montana State University

Sarah Lukes 9