

EELE 461/561 – Digital System Design

Module #1 – Digital Signaling

- **Topics**
 1. Course Overview
 2. Signaling Definitions
 3. Signal Composition
- **Textbook Reading Assignments**
 1. 1.1 – 1.7, 2.1, 2.10
- **What you should be able to do after this module**
 1. Describe what signal integrity is and why it is important
 2. Understand the terminology used in digital signaling
 3. Describe and use the risetime-bandwidth-product
 4. Describe the frequency components of a digital signal



Course Overview

- **Instructor:** Brock J. LaMeres
Office : 533 Cobleigh Hall
Phone : (406)-994-5987
Email : lameres@ece.montana.edu
Web : www.coe.montana.edu/ee/lameres/
- **Time / Location:** Lecture : Monday, Wednesday, Friday
9:00am – 9:50am
110 EPS
- **Textbook:** "Signal & Power Integrity Simplified",
Eric Bogatin,
Prentice Hall, 2nd edition 2009
- **Website:** www.coe.montana.edu/ee/lameres/courses/eele461_spring12
 - all handouts and homework are found on the website
 - it is your responsibility to download assignments



Course Overview

- **Office Hours:** Check instructor website for most recent hours
- **Requisites:** Pre-requisite EE308, EE334, EE371 (or consent of instructor)
- **Grading:**

Homework	- 25%
Exam #1	- 25%
Exam #2	- 25%
Final Project	- 25%

 - Homework Assignments are due at the beginning of class on indicated date.
 - Late homework will be accepted for one week after the due date with a penalty of 50% point reduction. No credit will be given for assignments over one week late.
 - No make up exams will be given. Plan on being available on the exam dates.



Course Overview

- **Final Project:**
 - A final design project will be assigned midway through the semester
 - the project will consist of a high speed link design including architecture, design, and simulation
 - a paper will be required that explains the design, its operation, simulation results, and layout
 - an in-class presentation will be required during the last week of the semester
 - you may work in teams of 2



Course Content

- **What is this course?**
 - We will look at how to design and analyze digital communication links in a wireline medium (i.e., conducting wires vs. wireless)
 - a communication link is the circuitry (Tx, Rx, and interconnect) used to transfer information between logical blocks
 - ex) uP to memory system or peripherals
 - computer-to-computer networking
 - We will look at the analog effects of a digital signal in order to understand how to design chip-to-chip communication links
 - We will learn how to create a noise budget that considers voltage and timing noise
 - We will see that the physical interconnect between IC's tends to limit the speed at which data can be transferred
 - We will also see that at modern integrated circuit speeds, interconnect needs to be treated as a transmission line (as opposed to just a simple capacitance)
 - We will learn to use modern CAD tools to help design and analyze these links



Course Content

- **What topics will be covered?**
 - 1) Signaling (Exam #1 Topics)
 - 2) Interconnect Analysis
 - 3) Interconnect Fabrication and Modeling
 - 4) Noise Sources & Budgeting
 - 5) Power distribution
 - 6) Link Architectures
 - 7) Measurement Techniques (Exam #2 Topics)
 - 8) Modern Bus Architectures
 - 9) Design Trade-offs



Course Content

Why do we need this course?


- We create all of our digital circuits using integrated circuit technology
- In order for two digital circuits to communicate information, the transmitter (Tx) sends a signal to the receiver (Rx).
- As long as the DC specifications are met at the Rx, the receiver can determine whether a 1 or 0 was sent.
- As long as sufficient time is allowed before and after the associated clock, the Rx flip-flops can latch and store the information that was sent.



Course Content

Why do we need this course?

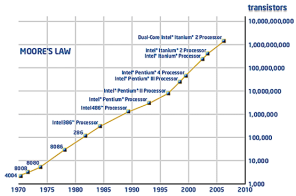
- So now all we need to do is meet DC and Timing specifications, and then go faster...
- In the beginning, integrated circuit performance was the limiting factor in going faster.



Course Content

Why do we need this course?

- We used to only care about the delay associated with the IC gates.
- On-chip and off-chip interconnect were modeled as capacitances, but they were secondary effects
- As we moved beyond $1\mu\text{m}$ process capability, the on-chip interconnect began to contribute more delay to the circuit than the gate itself
- Also at this time, the rise times of the IC drivers became fast enough so that off-chip interconnect (i.e., PCB's and cables) needed to be modeled as transmission lines.
- The mismatch in IC circuit performance and off-chip interconnect performance has to do with the manufacturing processes used (IC=photolithography/chemistry, Interconnect=chemistry/mechanical)

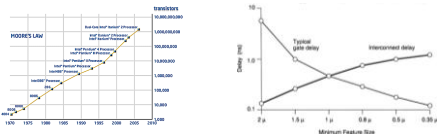

Course Content

Why do we need this course?

- Now, modern digital system speed is dominated by the interconnect between the integrated circuits making the Tx and Rx.
- The interconnect must be modeled not as simple wires, but as distributed capacitances, inductances, and impedances.
- This modeling also applies to the interconnect of the power distribution (i.e., V_{DD} and GND)
- We now have to consider the analog behavior of the signal as it travels through the interconnect to understand how fast and how robust a digital system can be.
- This course will present the techniques to design, model, analyze, and measure a modern digital system at the physical level.
- This type of design and analysis is also called

"Signal Integrity"



Course Content

Signal Integrity


- Signal integrity consists of 3 categories.
 - 1) Voltage Noise
 - sometimes just called *Noise*
 - what factors in the system eat into our Voltage Noise Margin
 - 2) Timing Noise
 - also called *Jitter*
 - the factors in the system eat into our Timing Margin
 - 3) Electromagnetic Interference (EMI)
 - when our system creates unwanted energy that interferes with the standards set by the Federal Communication Commission (FCC)



Signaling

Digital Signaling

Voltage Noise

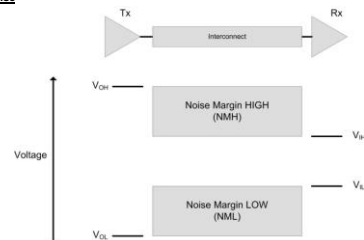

- what we're really after is a stable region between V_{H1} and V_{L1}




Signaling

Digital Signaling

Voltage Noise

- this area of Signal Integrity can further be sub-categorized into 4 distinct sources of noise:

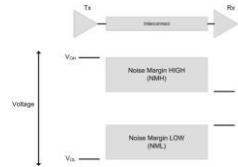
- 1) Single Net Quality
- 2) Cross-talk
- 3) Power Supply Quality
- 4) EMI



Signaling

Digital Signaling

Timing Noise

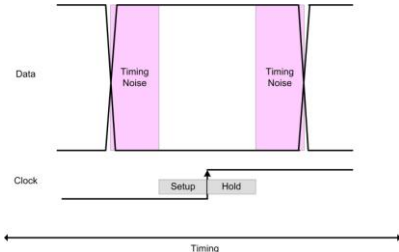

- we need to ensure that the data is stable long enough to meet the setup/hold specification of the Rx




Signaling

Digital Signaling

Timing Noise

- the entire timing of a signal can be broken down into 3 distinct parts:

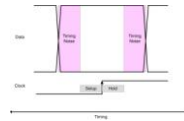- 1) Logical timing
 - i.e., the time for the gates to switch on chip
- 2) Interconnect Propagation
 - the time we have to wait for the signal to propagate
 - the time that we have to wait for any distortions to settle out
- 3) Receiver Setup/Hold
 - the time the data must remain stable around the receiver clock event



Signaling

Digital Signaling

Electromagnetic Interference

- The FCC sets standards for how much Electromagnetic energy can be transmitted in a given frequency band.
- Some of the bands are *licensed* (i.e., you have to pay to use them)
- If you make a product that isn't intended to use one of the FCC bands, you cannot inadvertently transmit energy into an FCC band above a certain level.
- This is considered *breaking the law* and you will not be able to ship your product if it does this.
- Products undergo EMI testing prior to shipping.
- As our systems go faster, it becomes easier for the energy to radiate out of our product because our small interconnect begins to look like an antenna




Signaling

Digital Signaling

Electromagnetic Interference (EMI)

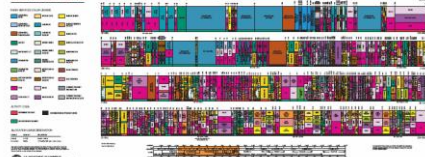
UNITED STATES FREQUENCY ALLOCATIONS THE RADIO SPECTRUM



Signaling

Digital Signaling

Eye Pattern

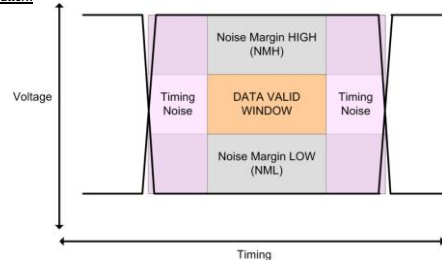


- we can combine the voltage and timing specifications into one diagram called an "Eye Pattern"



Signaling

Digital Signaling

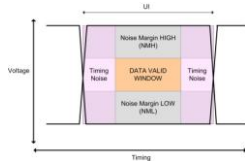Data Valid Window - the stable region in Voltage & Time around a timing event (i.e., a clock) that will guarantee a logic level is received



Unit Interval (UI) - the time between transitions on the data line

Max Data Rate - the fastest we can transmit information on the data line: $DR_{max} = \frac{1}{UI}$




Signaling

Digital Signaling

- in this class, we will learn how to create a *Noise Budget* that tabulates the contribution of each noise sources in our system.

- we can then predict if our system will reliably transmit data (i.e., does it work?) and how fast it can go.

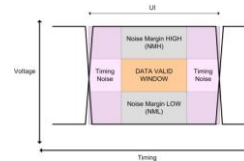- In order to do this, we must understand how to model and analyze the all of the components in a system (Tx, Interconnect, and Rx)



Signal Composition

A Digital Link

- A digital communication *link*, consists of 3 elements

- 1) A Driver (Tx)
- 2) Interconnect
- 3) A Receiver (Rx)



- The Driver and Receiver are constructed using Integrated Circuit Technology (ICs)

- The interconnect consists of all wires that connect the Tx and Rx. These include:

On-chip traces, package leads, PCB traces, connectors, and cables





Signal Composition

Driver Risetime

- The driver produces a digital edge

- We define the risetime (t_{rise}) as the time it takes for the edge to go from 10% of steady state to 90% of steady state.

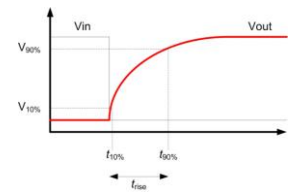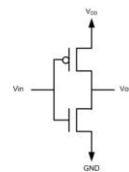- If the IC driver is NOT connected to any interconnect (on-chip or package), then the rise time will follow an RC exponential ramp where the R and C come from the Tx transistors.




Signal Composition

Risetime and Frequency

- The speed of the driver risetime is important because it tells us how fast we can possibly switch logic states (i.e., how fast of a frequency can be generated).

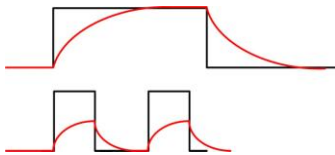- If we try to switch too fast, there isn't enough time for the rise time to get to its final value. This leads to data loss.



Signal Composition


Risetime and Frequency

- While the relative speed of the risetime to Period (T) is arbitrary, we can use a rule of thumb that it needs to be ~10% of the Fastest Period.

- We'll see how this is derived when we look at the Fourier Transform of a Square Wave

$$t_{rise} = (0.1) \cdot T_{min}$$
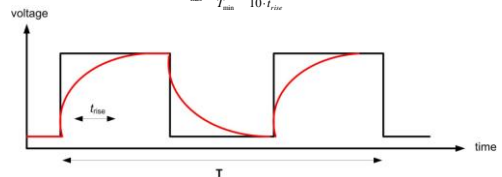
$$F_{max} = \frac{1}{T_{min}} = \frac{1}{10 \cdot t_{rise}}$$



Signal Composition

Risetime and Bandwidth

- Note that the driver rise time is NOT always what we get at the Receiver end of the interconnect



- We can think of this as a Linear Time Invariant (LTI) System where we have:

- 1) A forcing function, $x(t)$ (i.e., the driver edge and pattern)
- 2) A transfer function, $h(t)$ (i.e., the response of the interconnect)
- 3) The system output, $y(t)$ (i.e., what is seen at the Rx)




Signal Composition

Risetime and Bandwidth

- A very nice feature of an LTI system is that we can transform between the Time and Frequency domains easily.

- Not only do the functions transform, but so do operators.

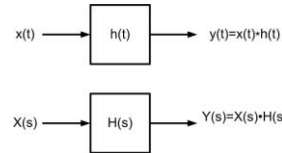- One of the main operator transforms that we take advantage of is *convolution* in the time domain becomes *multiplication* in the frequency domain.



Signal Composition

Risetime and Bandwidth

- We like to use the Frequency Domain because some things are easier to observe and some operations are easier.

- We are interested in what our forcing function looks like in the Frequency Domain because it tells us:

- 1) what spectrum of energy is stimulated in the system?
- 2) what bandwidth our interconnect needs in order to pass $X(s)$?
 - this helps us scale the cost of our materials and construction for the application.
 - i.e., we don't need to build a \$100k, 100GHz, PCB if we only stimulate 1GHz of spectral energy.
- 3) what bandwidth do our equivalent circuit models need to have?
 - higher frequency models take more simulation time to compute.
 - we want sufficient bandwidth for accuracy, but not too much that our simulations run longer than necessary.




Signal Composition

Risetime and Bandwidth

- Let's start by creating a rule of thumb that will allow us to easily switch between the Time and Frequency Domain for our RC Exponential Ramp.

- This is a relevant transform because this tends to be what CMOS edges look like.

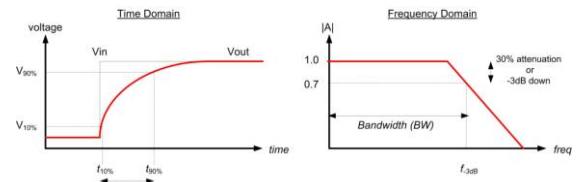
- First, let's define two metrics that we will use to describe the RC circuit.



Signal Composition

Risetime and Bandwidth

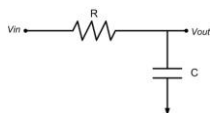- Let's solve the RC circuit and derive the expressions for risetime and bandwidth



$$V_{out}(s) = V_{in}(s) \cdot \left(\frac{\frac{1}{Cs}}{R + \frac{1}{Cs}} \right)$$

$$V_{out}(s) = V_{in}(s) \cdot \left(\frac{1}{1 + RCs} \right)$$



Signal Composition

Risetime and Bandwidth

- RC circuit cont...

We want to get this into a form so that we can use the Laplace Transform for an exponential approach.

Let's set $\alpha = 1/RC$

$$(1 - e^{-\alpha t}) \cdot u(t) \Leftrightarrow \frac{\alpha}{s(\alpha + s)}$$

Now let's plug in the transform for a unit step (1/s)

$$V_{out}(s) = V_{in}(s) \cdot \left(\frac{1}{1 + RCs} \right)$$

$$V_{out}(s) = V_{in}(s) \cdot \left(\frac{\frac{1}{RC}}{\left(\frac{1}{RC} \right) + s} \right)$$

$$V_{out}(s) = V_{in}(s) \cdot \left(\frac{\alpha}{\alpha + s} \right)$$

$$V_{out}(s) = \frac{\alpha}{s \cdot (\alpha + s)}$$



Signal Composition

Risetime and Bandwidth

- RC circuit cont...

Now we can transform into the time domain

$$V_{out}(s) = \frac{\alpha}{s - (\alpha + s)}$$

$$V_{out}(t) = (1 - e^{-\frac{t}{RC}}) \cdot u(t)$$

Now we can plug in $u(t)=1$ for $t>0$

$$V_{out}(t) = (1 - e^{-\frac{t}{RC}})$$

This is the generic Time Domain solution for an exponential ramp (i.e., a rising edge)



Signal Composition

Risetime and Bandwidth

- RC circuit cont...

Let's solve for the risetime. First $t_{10\%}$


$$0.1 = (1 - e^{-\frac{t_{10\%}}{RC}})$$

$$t_{10\%} = (0.1) \cdot RC$$

Then $t_{90\%}$

$$0.9 = (1 - e^{-\frac{t_{90\%}}{RC}})$$

$$t_{90\%} = (2.3) \cdot RC$$

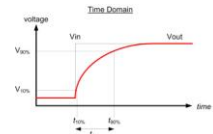

Finally, we solve for t_{rise}

$$t_{rise} = t_{90\%} - t_{10\%}$$

$$t_{rise} = (2.3) \cdot RC - (0.1) \cdot RC$$

$$t_{rise} = 2.2 \cdot RC$$



Signal Composition

Risetime and Bandwidth

- Let's now solve for Bandwidth in the Frequency Domain

We go back to an earlier form of the RC solution:

$$V_{out}(s) = V_{in}(s) \left(\frac{1}{1 + RCs} \right)$$



We are after the frequency at which the Magnitude of V_{out}/V_{in} is equal to 0.7.

$$\left| \frac{V_{out}(s)}{V_{in}(s)} \right| = \left| \frac{1}{1 + RCs} \right|$$

In a logarithmic scale, this attenuation can also be described as where the Amplitude is 3dB less than the Amplitude at DC.

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (RC\omega_{-3dB})^2}}$$

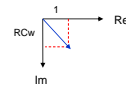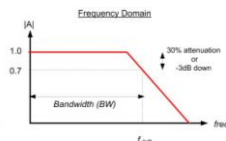We can use $1/\sqrt{2}$ to make the math come out easier since $(1/\sqrt{2} = 0.7)$.



Signal Composition

Risetime and Bandwidth

- RC circuit cont....

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (RC\omega_{-3dB})^2}}$$

Now we rearrange to solve for f_{-3dB}

$$\sqrt{2} = \sqrt{1 + (RC\omega_{-3dB})^2}$$

$$2 = 1 + (RC\omega_{-3dB})^2$$


$$1 = (RC\omega_{-3dB})^2$$

$$1 = RC\omega_{-3dB}$$

$$\omega_{-3dB} = \frac{1}{RC}$$

$$f_{-3dB} = \frac{1}{2\pi RC}$$

$$BW = \frac{1}{2\pi RC}$$

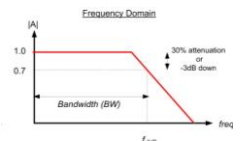

Signal Composition

Risetime Bandwidth Product

- We can relate the risetime to the bandwidth in what is known as the "Risetime Bandwidth Product"

$$t_{rise} = 2.2 \cdot RC$$

$$BW = \frac{1}{2\pi RC}$$

$$RC = \frac{t_{rise}}{2.2}$$

$$RC = \frac{1}{2\pi \cdot BW}$$

$$\frac{t_{rise}}{2.2} = \frac{1}{2\pi \cdot BW}$$

$$t_{rise} \cdot BW = \frac{2.2}{2\pi}$$

$$t_{rise} \cdot BW = 0.35$$



Signal Composition

Risetime Bandwidth Product

- We now have a quick expression to convert between key metrics in the Time and Frequency Domains for an RC circuit.

$$t_{rise} \cdot BW = 0.35$$

- This not only tells us how much bandwidth a passive network has, but also how much Spectral Energy is stimulated by a driver that outputs an exponential approach (i.e., an RC step)

ex) how much spectral energy is created by a driver with a 1ns step?

$$t_{rise} \cdot BW = 0.35$$

$$(1ns) \cdot BW = 0.35$$

$$BW = \frac{0.35}{1ns} = 350MHz$$




Signal Composition

• Risetime Bandwidth Product

- This expression also illustrates that as the risetime gets faster, higher frequencies are generated which makes sense...

$$t_{rise} \cdot BW = 0.35$$

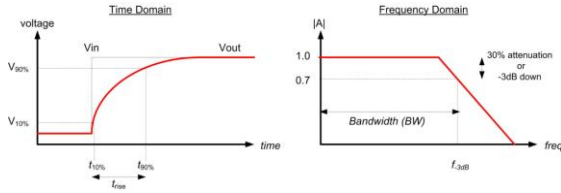


Signal Composition

• System Risetime & Bandwidth

- We found a very powerful and quick way to convert between a Time Domain metric (risetime) and a Frequency Domain metric (BW) using the *Risetime Bandwidth Product*.

- this was derived for a simple RC circuit, but we'll see it can be extended to a variety of step shapes.

$$t_{rise} \cdot BW = 0.35$$

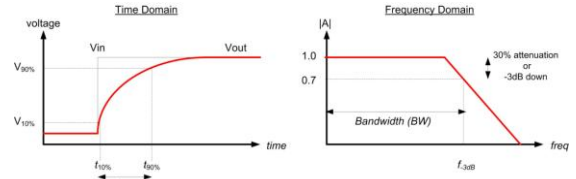

Signal Composition

• System Risetime & Bandwidth

- Note that this rule-of-thumb is used on a single element (i.e., a single driver, a single interconnect network, etc.)

- Remember that BW is when the sine wave at f-3dB is reduced to 70% of its value at steady state.

- Now we look at how to combine multiple elements to derive the *system risetime* of cascaded blocks

- We can combine multiple risetimes in a system to form the reduced equivalent system risetime using an RMS summation

$$t_{sys}^2 = t_{tx}^2 + t_{int}^2$$

OR

$$t_{sys} = \sqrt{t_{tx}^2 + t_{int}^2}$$



Signal Composition

• System Risetime & Bandwidth

- This expression can also be used on networks that have risetimes that aren't RC steps.

- This expression can be used if the system follows the *Central Limit Theorem*

- The *Central Limit Theorem* states:

the sum of independent, random variables approaches a normal distribution with squared standard deviations equal to the sum of squares of individual standard deviations regardless of individual distributions as long as each element's distribution:

- follows a Gaussian distribution (i.e., what you get if you differentiate the step)
- is symmetrical and uni-modal
- is continuous
- no one term dominates the expression



Signal Composition

• System Risetime & Bandwidth

- Let's see how we'd use this:

ex) We have a digital link with a driver outputting a risetime of 300ps. The interconnect system looks like an RC network with bandwidth of 2GHz. What is the risetime we would expect to see at the receiver?



- first convert the interconnect bandwidth to a risetime using the Risetime Bandwidth Product

$$t_{int} \cdot BW = 0.35$$

$$t_{int} \cdot (2GHz) = 0.35$$

$$t_{int} = 175ps$$

- now use the RMS sum to find the equivalent (or composite) risetime of the system.

$$t_{sys}^2 = t_{tx}^2 + t_{int}^2$$

$$t_{sys} = \sqrt{(300ps)^2 + (175ps)^2}$$

$$t_{sys} = 347ps$$



Signal Composition

• System Risetime & Bandwidth

- This can be expanded for as many elements that are in the system as long as they follow the *Central Limit Theorem*.

- Since risetime and bandwidth are inversely proportional, we can also use this technique for Bandwidths directly.

$$\frac{1}{BW_{sys}^2} = \frac{1}{BW_{tx}^2} + \frac{1}{BW_{int}^2}$$



Signal Composition

Square Waves

- Let's now look at the composition of a square wave.
- We are interested in the Frequency Domain representation of square waves because this a digital driver will ultimately output a data pattern which will have a square wave spectrum.
- We can visualize how much bandwidth a link will need to transmit a certain data pattern by looking at the data patterns spectrum.
- For now, let's assume that the risetime is instantaneous (we'll incorporate real risetimes at the end)



Signal Composition

Time and Frequency Domains

Frequency Domain Basics


- The Frequency Domain is completely made up by engineers and scientists. The only "Real" domain is the Time Domain.
- We create the Frequency Domain in order to visualize problems in a more intuitive manner.
- Also, some mathematical operations are easier in the Frequency Domain.
- The Frequency Domain **only contains Sine Waves**
- We represent a single Sine wave with a dot or line representing its Frequency and Amplitude
- We can put phase on a 3rd axis, or on a different plot



Signal Composition

Time and Frequency Domains

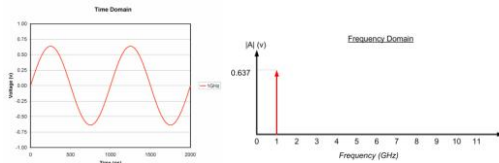- data in the Frequency Domain contains the same information as the Time Domain, but in *less space*



- DC offset information for a waveform is represented in the Frequency Domain by placing magnitude information at **0 Hz**



Signal Composition

Time and Frequency Domains

- Fourier Analysis tells us that any repetitive waveform in the Time Domain can be represented by one or more sine waves in the Frequency Domain.
- When a waveform is created using more than one sine wave, we say it has a Frequency Spectrum
- We can *Transform* back and forth between the domains using the *Fourier Transform*
- The *Fourier Integral* will transform any repetitive function:

Time to Frequency Domain

$$X(f) = \int_{-\infty}^{+\infty} x(t) \cdot e^{-j2\pi ft} dt$$

Frequency to Time Domain

$$x(t) = \int_{-\infty}^{+\infty} X(f) \cdot e^{j2\pi ft} df$$



Signal Composition

Time and Frequency Domains

Discrete Fourier Transform (DFT)

- In the real world, we perform this transformation on discrete points of the function.
- The number of points is fixed prior to the transform.
- The pattern is assumed to repeat indefinitely every T seconds.
- This is called a **Discrete Fourier Transform (DFT)**.

Fast Fourier Transform (FFT)

- A special case of the DFT is when the number of points is a power of 2 (256, 512, 1024, ...)
- This special case enables the Matrix Math to be sped up considerably.
- This is called a **Fast Fourier Transform (FFT)** and is the most common algorithm used today.
- The FFT can be 100-10,000 times faster than a general DFT.



Signal Composition

Fourier Transform of Square Waves

- One way to construct the Fourier Transform of a Square Wave is to construct the Square Wave using multiple, basic functions.
- The Fourier Transform not only allows functions to be transformed, but also operations.
- This means we can construct a complex expression for a waveform, and then transform the individual parts and operations.
- There are two common operations that we use when looking at Square Waves

Fourier Transform of Operations

Operation

"Scaling"

"Convolution"

Time Domain

$f(at)$

$f(t) * g(t)$

Frequency Domain

$\frac{1}{|a|} F\left(\frac{f}{a}\right)$

$F(f) \cdot G(f)$




Signal Composition

Fourier Transform of Basic Functions

Rectangle Function $\Pi(t)$

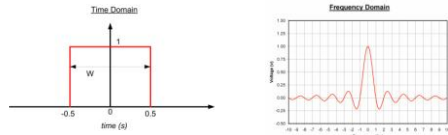- A Rectangle Function is a pulse with unit width and height.
- We can use this to represent a single pulse of a square wave with a finite pulse width (W).
- This transforms into the *sinc* function with zero crossings at integer multiples of $1/W$.



Function: $\Pi(t)$

$\text{sinc}(f)$




Signal Composition

Fourier Transform of Basic Functions

Shaw Function $\text{III}(t)$

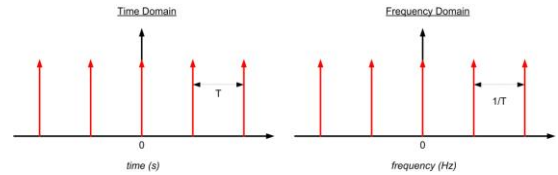- A Shaw Function is an infinite series of impulse functions.
- This functions transforms into another Shaw function in the Frequency Domain



Functions: $\text{III}(t)$

$\text{III}(f)$



Signal Composition


Fourier Transform of Basic Functions

Square Wave

- In the Time Domain, if we convolve a Rectangle Function with a Shaw Function, we will get a repetitive sequence of pulses.
- If W is set to $T/2$, then we will have a 50% duty cycle square wave (a special case).




Signal Composition

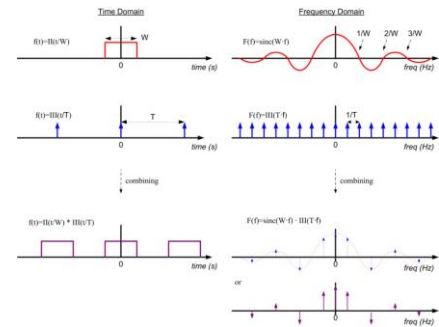

Signal Composition

Fourier Composition of a Square Wave


- Notice that when we have a 50% duty cycle, the *sinc* envelope eliminates all even harmonics.
- We are left with only the DC offset, the Fundamental Frequency, and Odd Harmonics.
- This is what most people are familiar with when they talk about the Fourier spectrum of a square wave.
- However, this illustrates that if we alter the duty cycle, we **WILL** start getting even harmonics due to the *sinc* function spreading out.

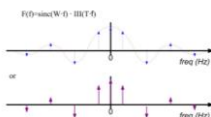

Signal Composition

Fourier Composition of a Square Wave

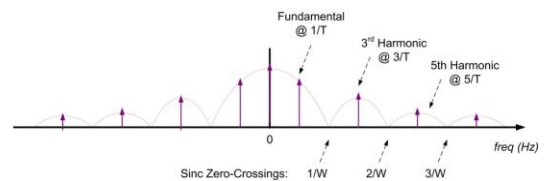
- if we only concern ourselves with the Magnitude, we get the more familiar Fourier Spectrum.
- Note that a smaller pulse increases the width of the *sinc* envelope
- The amplitude of the spikes of energy at each multiple of the fundamental frequency depend the shape of the *sinc* envelope.



Signal Composition

Fourier Composition of a Square Wave

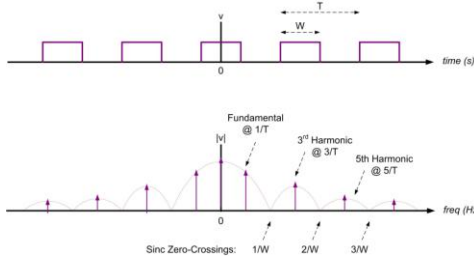- We now have a transform for an Ideal Square Wave



Signal Composition

Fourier Composition of a Square Wave

- We now have two uses for the word "Frequency".

- We use *Frequency* to describe the rate at which the digital square wave toggles.
- We also use *Frequency* to describe the harmonics that make up the square wave.

- To distinguish the two, we typically use the term *Toggle Rate* or *Toggle Frequency* for the time domain square wave.

$$F_{toggle} = \frac{1}{T_{square, wave}} = \frac{1}{T_{toggle}}$$

- But we still sometimes use the word *frequency* when we discuss digital signals, so we always need to be aware of the difference between *Toggle Frequency* and the frequency of the Square Wave's *Spectral Content*.

Signal Composition

Fourier Composition of a Square Wave

- What the Frequency Domain shows us is that the Square wave is made up of a series of sine waves with different amplitudes and frequencies that are at harmonic multiples of the fundamental.

- An ideal square wave is made up of only the ODD harmonics of the fundamental frequency.

- A square wave with less than 50% duty cycle begins to include EVEN harmonics due to the *sinc* envelope expanding.

- The amplitude of each harmonic is given by:

$$A_n = \frac{2}{\pi \cdot n}$$

where n is the harmonic number (i.e., 1, 3, 5, 7, etc...)

Signal Composition

Fourier Composition of a Square Wave

- An ideal square wave will have amplitudes that get smaller and smaller as the harmonic frequency goes up.

$$A_n = \frac{2}{\pi \cdot n}$$

Ex) a 1v square wave ($V_{LOW} = -0.5v$, $V_{HIGH} = +0.5v$) will be made up of sine waves with Amplitudes:


	Amplitude
Fundamental	0.637 v
3 rd	0.212 v
5 th	0.127 v
7 th	0.091 v
9 th	0.071 v
11 th	0.058 v

- notice that the higher the frequency, the less amplitude that the harmonic contributes to the reconstruction of the Square Wave.

Signal Composition

Fourier Composition of a Square Wave

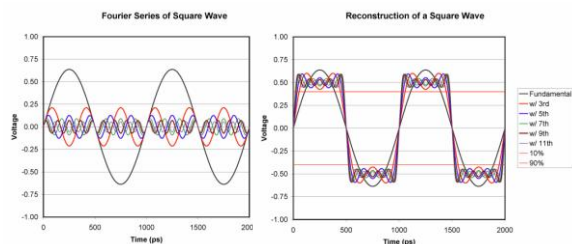- if we split out the sine waves in the Time Domain, we can see the individual components:




Signal Composition

Fourier Composition of a Square Wave

- Notice that as we add more harmonics to the fundamental, we get a waveform that looks more and more like an ideal square wave.

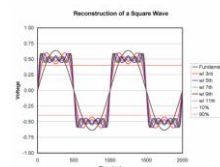- If we add all the harmonics (up to infinity), we will get a perfect square wave with instantaneous risetimes.




Signal Composition

Fourier Composition of a Square Wave

- However, we know that no system can output or transmit infinite frequency.
- The big question for digital system designers becomes...

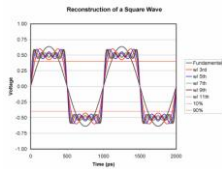"How many harmonics do I need to get a square wave that is good enough?"




Signal Composition

Fourier Composition of a Square Wave

- This is an arbitrary question and depends on how fast of a risetime each system needs.
- But, we can tie this question back to one of our rules-of-thumbs relating the risetime to the period of the square wave.
- earlier we stated that the risetime should be ~10% of the period

$$t_{rise} \leq (0.1) \cdot T_{toggle}$$

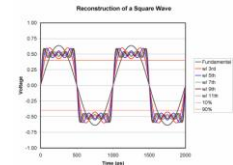


Signal Composition

Fourier Composition of a Square Wave

- Let's start with only the fundamental frequency and see what percentage of the period that the risetime takes.

- Then we'll add harmonics and see how it changes: $\% \text{ of } T_{toggle} = \left(\frac{t_{rise}}{T_{toggle}} \right) \times 100$


Square Wave Composition	$(t_{rise}/T_{period})\%$
Fundamental	22%
Fund + 3 rd	11%
Fund + 3 rd + 5 th	7.4% **
Fund + 3 rd + 5 th + 7 th	5.7%
Fund + 3 rd + 5 th + 7 th + 9 th	4.4%
Fund + 3 rd + 5 th + 7 th + 9 th + 11 th	3.6%

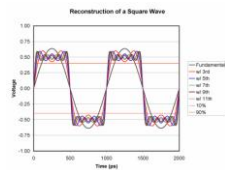

Signal Composition

Fourier Composition of a Square Wave

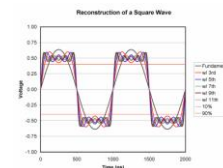- This tells us that if we include the fundamental + 3rd harmonic, the square wave risetime is 11% of the period.
- If we include the 5th, this goes down to 7.4%, which meets our objective.
- So we can say that we really should try to get the 5th harmonic of the square wave in order to reconstruct a reasonable representation.



Signal Composition

Fourier Composition of a Square Wave

- How does this all compare to the *Risetime Bandwidth Product*?
- Remember our original expression was derived for a single-pole, RC circuit $t_{rise} \cdot BW = 0.35$
- If we look at the risetime bandwidth product of a Square Wave made up of a Fourier Series of sine waves, we get:

Spectral Content	Risetime Bandwidth Product
Fundamental	0.21
Fund + 3 rd	0.33
Fund + 3 rd + 5 th	0.37 ***
Fund + 3 rd + 5 th + 7 th	0.4
Fund + 3 rd + 5 th + 7 th + 9 th	0.4
Fund + 3 rd + 5 th + 7 th + 9 th + 11 th	0.4

NOTE: The BW we use is the frequency of the highest harmonic present in the spectrum of the square wave.

- the product is pretty close to 0.35, especially if we try to include up to the 5th harmonic.



Signal Composition

Fourier Composition of a Square Wave

- This also shows that for different shaped risetimes, we can simply change the risetime BW product to get more accurate results
 - RC step, use 0.35
 - Gaussian step, use 0.4
- BUT REMEMBER, this is an approximation to get a *gut-feel*. So we don't need to get too hung up on the exact number as long as it is around 0.35.
- One more nice thing is that the Fourier Series Representation has a Gaussian Distribution by nature, which means it follows the Central Limit Theorem.
- That means that even if we choose to use 0.4 in our risetime BW product, we can still use a sum-of-squares expression to describe the composite risetime.



Signal Composition

- **Fourier Composition of a Square Wave**

- Once again, remember that we are talking about the stimulated energy of the driver.
- What gets to the Receiver in our digital link is another story.
- At first glance, we think this is pretty straight forward because an interconnect system will simply attenuate the forcing function's harmonics.
- In reality, when we look at the distributed nature of an interconnect system, we see that reflections can actually cause the harmonics to be *amplified*!!
- this makes the analysis a little more interesting.
- Next, we look how to model the interconnect in order to understand how its response will effect the wave shape of the forcing function.

